



Department of Electrical and Electronic Engineering
Level-I, Term-I

Mid Term Examination, Spring-2023

Course Code: EEE 111

Course Title: Electrical Circuits I

Notes:

Time: 1 Hour

- Each question carries 30 marks.
- Figure on the right of each question indicate marks for respective question.
- Answer any two questions including question no.-1

Full Marks: 60

- From the following data table, determine the resistance of each device and discuss on which device conductivity level is higher. Consider, resistivity $\rho = 1\Omega m$ for all devices. (10)

Device	Length, l (m)	Area, A (m^2)
A	1	0.52
B	2	0.96
C	3	1.5
D	4	1.01
E	5	0.83

- Determine the voltage v_o and the current i in the circuit given in Fig. 1(b). (15)

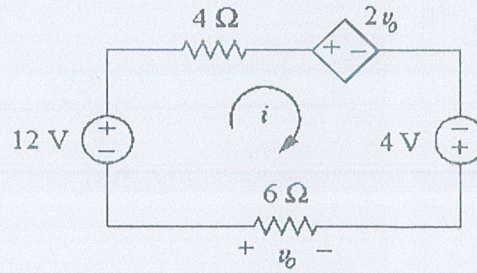


Fig. 1(b)

- Show That, $P = VI$ (5)
[Here, symbols are indicating the usual meaning]
- A house has the following electrical appliance usage: (20)
 - Two 9-watt fluorescent lamp used for 4 hours per day
 - One 60-watt fan used for 2 hours per day
 - One 0.75 kilo-watt refrigerator that runs 24 hours per day with compressor that runs 12 hours and remains off 12 hours.
 - One 0.6 hp water pump used 30 minutes per day.If the per unit cost 7tk, determine the *cost of January, 2022 to February, 2022.*

- b. Determine the resistance R_{eq} seeing into the terminal a-b given in Fig. 2 (b) (10)

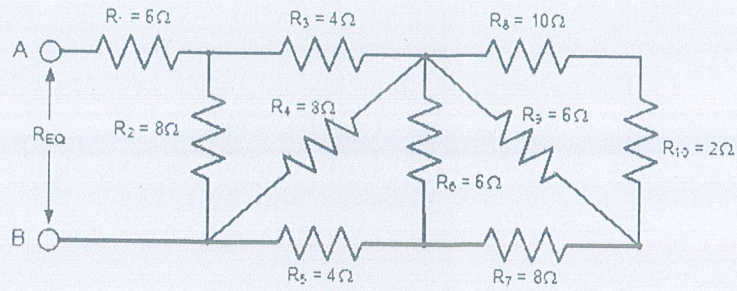


Fig. 2 (b)

3. a. Derive *Ohm's Law* (5)

- b. Derive the parallel resistance and current divider rule of the following circuit in Fig. 3(b): (15)

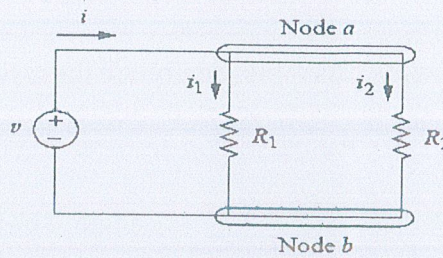


Fig. 3(b)

- c. Using Voltage divider rule find the voltage drop of all branches of the following circuit in Fig. 3 (c), also show that, supply voltage = drop voltage (10)

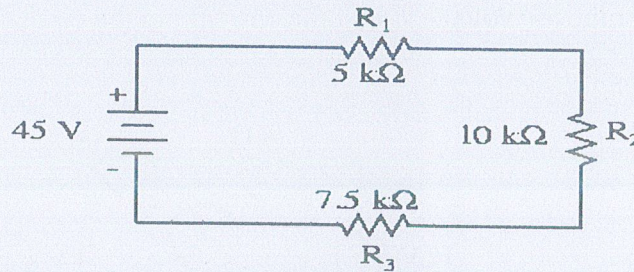


Fig. 3(c)