
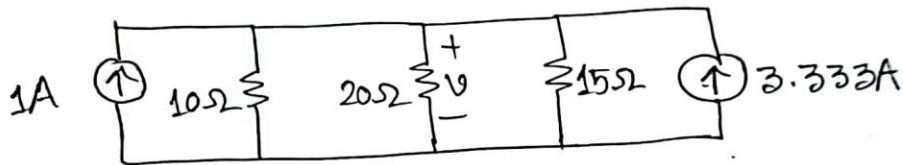



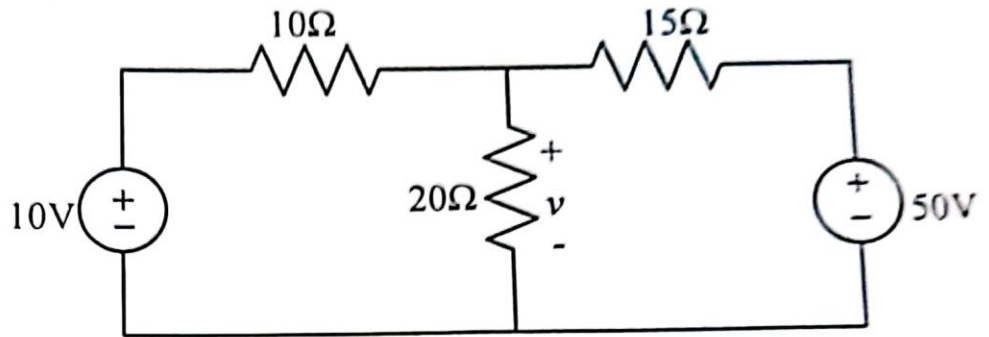
1. Using source transformation, find v in the following circuit. [5]



$$i = \frac{4.333\text{A}}{(6+20)\Omega} \times 6\Omega = 0.999\text{A}$$

$$v = 20i = 20 \times 0.999 = 19.98\text{V} = 20\text{V}$$

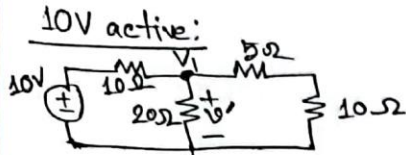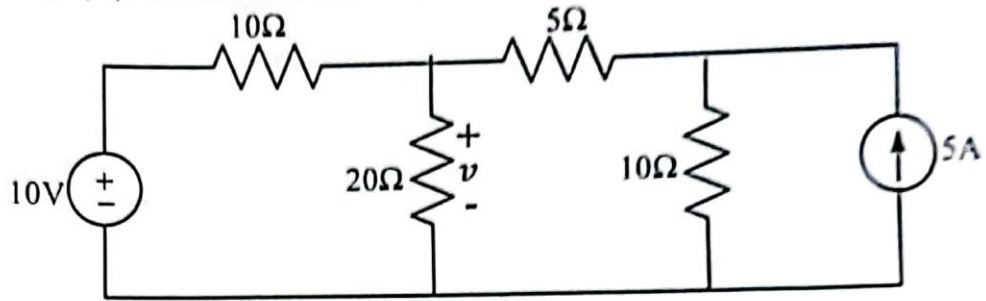2. Using superposition theorem, find v in the following circuit. [5]



KCL at Node 1:

$$\frac{v_1 - 10}{10} + \frac{v_1}{20} + \frac{v_1}{15} = 0$$


$$v_1 \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{15} \right) = 1$$

$$0.217 v_1 = 1$$

$$v_1 = 4.615 \text{ V}$$

$$\therefore v' = v_1 = 4.615 \text{ V}$$

5A active:

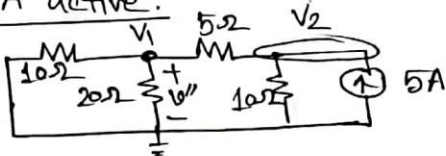

KCL at Node 1:

$$\frac{v_1 - v_2}{5} + \frac{v_1}{20} + \frac{v_1}{10} = 0$$

$$v_1 \left(\frac{1}{5} + \frac{1}{20} + \frac{1}{10} \right) + v_2 \left(-\frac{1}{5} \right) = 0$$

$$0.35 v_1 - 0.2 v_2 = 0 \quad \text{--- (I)}$$

KCL at Node 2:

$$\frac{v_2 - v_1}{5} + \frac{v_2}{10} = 5$$

$$v_1 \left(-\frac{1}{5} \right) + v_2 \left(\frac{1}{5} + \frac{1}{10} \right) = 5$$

$$-0.2 v_1 + 0.3 v_2 = 5 \quad \text{--- (II)}$$

$$v_1 = 15.385 \text{ V}$$

$$v_2 = 26.923 \text{ V}$$

$$\therefore v'' = v_1 = 15.385 \text{ V}$$

$$\therefore v = v' + v''$$

$$= 4.615 + 15.385 = 20 \text{ V}$$