

BANGLADESH ARMY INTERNATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY (BAIUST), CUMILLA

Term Final Examination, Spring 2024

Department of Computer Science and Engineering (CSE)

Level-1, Term-1

Course Code: EEE 111

Course Title: Electrical Circuit Analysis

Credit Hour: 03

Full Marks: 150

Time: 2 hr

ANSWER SHEET

A1. i. Discuss the "Norton's theorem" how can be used to solve a linear circuit with necessary diagrams and examples.

Norton's Theorem Discussion

Statement Norton's Theorem states that any two-terminal linear electrical circuit can be replaced by an equivalent circuit consisting of a single **current source I_N** in parallel with a single **resistor R_N** .

- The Norton Current, I_N (or short-circuit current, I_{sc}), is the current flowing through a short circuit placed across the two terminals.
- The Norton Resistance, R_N , is the equivalent resistance looking back into the two terminals when all independent voltage sources are short-circuited and all independent current sources are open-circuited. (Note: R_N is the same as the Thevenin Resistance, R_{Th}).

Procedure for Using Norton's Theorem To find the Norton equivalent circuit at terminals $a - b$:

1. **Find the Norton Current (I_N):** Short the terminals $a - b$ and calculate the current I_{sc} flowing through the short circuit. This current is I_N .
2. **Find the Norton Resistance (R_N):** Turn off all independent sources (replace voltage sources with short circuits and current sources with open circuits). Calculate the equivalent resistance R_{eq} looking into the terminals $a - b$. This resistance is R_N .

This is an exclusive content of Academizz. To get access to more resources, subscribe to Academizz(app.academizz.com).

3. **Construct the Equivalent Circuit:** Draw the Norton equivalent circuit with the current source I_N in parallel with the resistor R_N .
4. **Connect the Load:** Reconnect the original load (if any) across the terminals $a-b$ and analyze the resulting circuit.

Diagrams (Placeholders) Figure showing the Norton Equivalent Circuit: I_N in parallel with R_N .

A1. ii. Derive the voltage equation of a capacitor and the equation of energy stored in the capacitor.

Voltage Equation of a Capacitor

The fundamental relationship between current $i(t)$ and voltage $v(t)$ for a capacitor with capacitance C is:

$$i(t) = C \frac{dv(t)}{dt}$$

To find the voltage $v(t)$, we integrate the current $i(t)$ over time. First, rearrange the equation:

$$\frac{dv(t)}{dt} = \frac{1}{C} i(t)$$

Integrate both sides from an initial time t_0 to an arbitrary time t :

$$\int_{t_0}^t \frac{dv(\tau)}{d\tau} d\tau = \int_{t_0}^t \frac{1}{C} i(\tau) d\tau$$

Applying the Fundamental Theorem of Calculus to the left side:

$$v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

Solving for the voltage $v(t)$:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

Where $v(t_0)$ is the initial voltage across the capacitor at time t_0 .

Energy Stored in a Capacitor

The instantaneous power $P(t)$ absorbed by the capacitor is the product of voltage and current:

$$P(t) = v(t)i(t)$$

The energy $W(t)$ stored in the capacitor is the integral of the power over time. Assuming the capacitor was uncharged at $t = -\infty$ (i.e., $v(-\infty) = 0$):

$$W(t) = \int_{-\infty}^t P(\tau) d\tau = \int_{-\infty}^t v(\tau)i(\tau) d\tau$$

Substitute the current equation $i(t) = C \frac{dv(t)}{dt}$:

$$W(t) = \int_{-\infty}^t v(\tau) \left(C \frac{dv(\tau)}{d\tau} \right) d\tau$$

Change the variable of integration from time τ to voltage v :

$$W(t) = C \int_{v(-\infty)}^{v(t)} v dv$$

Since $v(-\infty) = 0$:

$$W(t) = C \int_0^{v(t)} v dv$$

Evaluate the integral:

$$W(t) = C \left[\frac{v^2}{2} \right]_0^{v(t)} = C \left(\frac{v^2(t)}{2} - 0 \right)$$

The equation for the energy stored in the capacitor is:

$$W(t) = \frac{1}{2} C v^2(t)$$

A2. i. Apply the superposition theorem to find v_0 in the circuit of Figure A2.(ia) and Figure A2.(ib).

Circuit A2.(ia)

The circuit has two independent sources: a 6 A current source and an 18 V voltage source. v_0 is the voltage across the 1Ω resistor. The two 2Ω resistors are in parallel, and their equivalent resistance $R_p = 2\Omega || 2\Omega = 1\Omega$. This R_p is in series with the 1Ω resistor where v_0 is measured, forming a total series resistance $R_{series} = 1\Omega + 1\Omega = 2\Omega$.

Case 1: 6 A source active, 18 V source shorted (v'_0)

1. The 18 V source is replaced by a short circuit. The 4Ω resistor is now in parallel with $R_{series} = 2\Omega$.
2. The total 6 A current splits between $R_{series}(2\Omega)$ and $R_{4\Omega}(4\Omega)$.
3. Current through the R_{series} branch (I'), using the Current Divider Rule:

$$I' = 6 \text{ A} \times \frac{R_{4\Omega}}{R_{series} + R_{4\Omega}} = 6 \text{ A} \times \frac{4\Omega}{2\Omega + 4\Omega} = 6 \text{ A} \times \frac{4}{6} = 4 \text{ A}$$

4. This current flows through the 1Ω resistor, establishing v'_0 :

$$v'_0 = I' \times 1\Omega = 4 \text{ A} \times 1\Omega = 4 \text{ V}$$

Case 2: 18 V source active, 6 A source open (v''_0)

1. The 6 A source is replaced by an open circuit.
2. The total resistance in the loop is the series combination of 4Ω and R_{series} :

$$R_{total} = 4\Omega + 2\Omega = 6\Omega$$

3. The current flowing from the 18 V source (I''):

$$I'' = \frac{18 \text{ V}}{R_{total}} = \frac{18 \text{ V}}{6\Omega} = 3 \text{ A}$$

4. This current flows through the 1Ω resistor, establishing v''_0 :

$$v''_0 = I'' \times 1\Omega = 3 \text{ A} \times 1\Omega = 3 \text{ V}$$

Total Voltage v_0

$$v_0 = v'_0 + v''_0 = 4 \text{ V} + 3 \text{ V} = 7 \text{ V}$$

Circuit A2.(ib)

The circuit has three independent sources connected to the common node v_0 : a 5 A current source, a 9 V voltage source, and a 3 V voltage source.

Case 1: 5 A source active, 9 V shorted, 3 V shorted (v'_0)

1. Deactivate voltage sources (short circuits). The three parallel branches have resistances 4Ω , 3Ω , and 1Ω .
2. Apply KCL at node v'_0 :

$$\begin{aligned}I_{\text{in}} &= I_{4\Omega} + I_{3\Omega} + I_{1\Omega} \\5 &= \frac{v'_0}{4} + \frac{v'_0}{3} + \frac{v'_0}{1} \\5 &= v'_0 \left(\frac{1}{4} + \frac{1}{3} + 1 \right) = v'_0 \left(\frac{3 + 4 + 12}{12} \right) = v'_0 \frac{19}{12} \\v'_0 &= \frac{5 \times 12}{19} = \frac{60}{19} \text{ V}\end{aligned}$$

Case 2: 9 V source active, 5 A open, 3 V shorted (v''_0)

1. Deactivate 5 A (open circuit) and 3 V (short circuit).
2. The circuit is now a parallel connection of 4Ω , a branch with 3Ω and 9 V (pos up), and 1Ω .
3. Apply KCL at node v''_0 :

$$\frac{v''_0}{4} + \frac{v''_0 - 9}{3} + \frac{v''_0}{1} = 0$$

Multiply by 12:

$$\begin{aligned}3v''_0 + 4(v''_0 - 9) + 12v''_0 &= 0 \\3v''_0 + 4v''_0 - 36 + 12v''_0 &= 0 \implies 19v''_0 = 36 \\v''_0 &= \frac{36}{19} \text{ V}\end{aligned}$$

Case 3: 3 V source active, 5 A open, 9 V shorted (v'''_0)

1. Deactivate 5 A (open circuit) and 9 V (short circuit).
2. The circuit is a parallel connection of 4Ω , 3Ω , and a branch with 1Ω and 3 V (pos up).

3. Apply KCL at node v_0''' :

$$\frac{v_0'''}{4} + \frac{v_0'''}{3} + \frac{v_0''' - 3}{1} = 0$$

Multiply by 12:

$$3v_0''' + 4v_0''' + 12(v_0''' - 3) = 0$$

$$3v_0''' + 4v_0''' + 12v_0''' - 36 = 0 \implies 19v_0''' = 36$$

$$v_0''' = \frac{36}{19} \text{ V}$$

Total Voltage v_0

$$v_0 = v_0' + v_0'' + v_0''' = \frac{60}{19} + \frac{36}{19} + \frac{36}{19} = \frac{60 + 36 + 36}{19} = \frac{132}{19} \text{ V}$$

$$v_0 = \frac{132}{19} \text{ V} \approx 6.947 \text{ V}$$

A2. ii. Obtain the Norton equivalent of the circuit in Figure A2.(ii) to the left of terminals a – b. Use the result to find current i. (10 Marks)

The circuit to the left of terminals $a - b$ is a source network. The load is the 5Ω resistor, and i is the current flowing through it.

Step 1: Find Norton Resistance (R_N)

Deactivate all independent sources:

- 2 A current source is replaced by an ****open circuit****.
- 12 V voltage source is replaced by a ****short circuit****.

Looking into terminals $a - b$:

- The 4Ω resistor is connected between the common node V_L and terminal b .
- The 6Ω resistor is connected between terminal a and node V_L (since the 12 V source is shorted).
- The open circuit from the 2 A source is in parallel with the 4Ω resistor.

Thus, $R_{6\Omega}$ and $R_{4\Omega}$ are in series between a and b :

$$R_N = 6\Omega + 4\Omega = 10\Omega$$

Step 2: Find Norton Current (I_N)

Short the terminals $a - b$ and calculate the short-circuit current I_{sc} flowing from a to b . Let $V_b = 0$ and $V_a = 0$. Apply Nodal Analysis at the common node V_L (left of 6Ω and 4Ω). KCL at V_L :

$$I_{2A} = I_{4\Omega} + I_{6\Omega}$$
$$2 = \frac{V_L - 0}{4} + \frac{V_L - 12 - 0}{6}$$

Multiply by 12:

$$24 = 3V_L + 2(V_L - 12)$$

$$24 = 5V_L - 24 \implies 5V_L = 48 \implies V_L = \frac{48}{5} = 9.6 \text{ V}$$

The short circuit current I_{sc} is the current flowing from a to b through the 6Ω branch (where i is defined down).

$$I_N = I_{sc} = I_{6\Omega} = \frac{V_a - (V_L - 12 \text{ V})}{6\Omega} \quad (\text{Current from } a \text{ to } V_L)$$

$$I_N = \frac{0 - (9.6 - 12)}{6} = \frac{2.4}{6} = 0.4 \text{ A}$$

The positive sign means I_N flows from a to b .

$$I_N = \mathbf{0.4 \text{ A}}$$

Step 3: Find Current i in 5Ω Load

The load resistance is $R_L = 5\Omega$. The current i is the current through R_L . Use the Current Divider Rule in the Norton equivalent circuit:

$$i = I_N \times \frac{R_N}{R_N + R_L}$$

$$i = 0.4 \text{ A} \times \frac{10\Omega}{10\Omega + 5\Omega} = 0.4 \times \frac{10}{15} = 0.4 \times \frac{2}{3}$$

$$i = \frac{0.8}{3} = \frac{\mathbf{4}}{\mathbf{15}} \text{ A} \approx \mathbf{0.2667 \text{ A}}$$

The current i flows $\mathbf{0.2667 \text{ A}}$ downwards from a to b .

A3. i. Use source transformations to reduce the circuit in Figure A3.(i) to a single voltage source in series with a single resistor.

The circuit in Figure A3.(i) consists of three parallel branches. We will convert each branch to a Norton equivalent (current source in parallel with a resistor) to find the total Norton equivalent, and then transform it to the Thevenin equivalent (voltage source in series with a resistor). Let the top node be V_A and the bottom node be V_B (reference).

Step 1: Determine Norton Equivalent Resistance (R_N)

Deactivate all independent sources: the 3 A current source is open-circuited, and the 12 V and 16 V voltage sources are short-circuited. The three resistors (10Ω , 20Ω , 40Ω) are now in parallel.

$$R_N = 10\Omega || 20\Omega || 40\Omega$$
$$\frac{1}{R_N} = \frac{1}{10} + \frac{1}{20} + \frac{1}{40} = \frac{4 + 2 + 1}{40} = \frac{7}{40}$$
$$R_N = \frac{40}{7}\Omega \approx 5.714\Omega$$

The equivalent series resistance (R_{Th}) is equal to R_N .

$$R_{Th} = \frac{40}{7}\Omega$$

Step 2: Determine Norton Current (I_N)

The total Norton current I_N is the algebraic sum of the individual equivalent Norton currents (I_{N1} , I_{N2} , I_{N3}). We assume the current direction is positive when flowing UP (into node V_A).

1. **Branch 1 (3 A source || 10Ω):** The current source is flowing up.

$$I_{N1} = 3 \text{ A}$$

2. **Branch 2 (12 V source in series with 20Ω):** We assume the 12 V source polarity is consistent with the 3 A source (positive terminal towards V_A based on Nodal consistency).

$$I_{N2} = \frac{12 \text{ V}}{20\Omega} = 0.6 \text{ A} \quad (\text{Flowing up})$$

3. **Branch 3 (16 V source in series with 40Ω):** Similarly, assume the 16 V source is oriented positive towards V_A .

$$I_{N3} = \frac{16 \text{ V}}{40\Omega} = 0.4 \text{ A} \quad (\text{Flowing up})$$

Total Norton Current (I_N flowing up):

$$I_N = I_{N1} + I_{N2} + I_{N3} = 3 \text{ A} + 0.6 \text{ A} + 0.4 \text{ A} = 4.0 \text{ A}$$

Step 3: Determine Thevenin Voltage (V_{Th})

The Thevenin voltage is $V_{Th} = I_N \times R_N$.

$$V_{Th} = 4 \text{ A} \times \frac{40}{7}\Omega = \frac{160}{7} \text{ V}$$

Result The circuit is reduced to a single voltage source V_{Th} in series with a single resistor R_{Th} :

$$V_{Th} = \frac{160}{7} \text{ V} \approx 22.86 \text{ V}$$

$$R_{Th} = \frac{40}{7} \Omega \approx 5.71 \Omega$$

A3. ii. The variable resistor R in Figure A3.(ii) is adjusted until it absorbs the maximum power from the circuit. Calculate the value of R for maximum power. Determine the maximum power absorbed by R.

We need to find the Thevenin equivalent circuit across the terminals of R .

Step 1: Calculate Thevenin Resistance (R_{Th})

Replace the 40 V voltage source with a short circuit. The circuit becomes a parallel combination of two series branches:

- **Upper Branch:** $80\Omega + 20\Omega = 100\Omega$
- **Lower Branch:** $10\Omega + 90\Omega = 100\Omega$

R_{Th} is the parallel combination of these two branches:

$$R_{Th} = 100\Omega || 100\Omega = \frac{100 \times 100}{100 + 100} = 50\Omega$$

Value of R for Maximum Power According to the Maximum Power Transfer Theorem:

$$R = R_{Th} = 50\Omega$$

Step 2: Calculate Thevenin Voltage (V_{Th})

V_{Th} is the open-circuit voltage across the terminals where R was connected ($V_a - V_b$). The 40 V source is applied across the left-side internal nodes. Due to the two series loops on the bridge, the currents are:

- **Upper Loop Current (I_{up}):** $I_{up} = \frac{40 \text{ V}}{80\Omega + 20\Omega} = 0.4 \text{ A}$
- **Lower Loop Current (I_{down}):** $I_{down} = \frac{40 \text{ V}}{10\Omega + 90\Omega} = 0.4 \text{ A}$

The voltage at node a (V_a) is the voltage drop across the 20Ω resistor, and the voltage at node b (V_b) is the voltage drop across the 90Ω resistor (assuming the source is connected between the common nodes V_C and V_D , and we measure V_a and V_b with respect to V_D).

$$V_a = I_{up} \times 20\Omega = 0.4 \text{ A} \times 20\Omega = 8 \text{ V}$$

$$V_b = I_{down} \times 90\Omega = 0.4 \text{ A} \times 90\Omega = 36 \text{ V}$$

$$V_{Th} = V_a - V_b = 8 \text{ V} - 36 \text{ V} = -28 \text{ V}$$

The magnitude of V_{Th} is 28 V.

Step 3: Calculate Maximum Power (P_{max})

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$P_{max} = \frac{(28 \text{ V})^2}{4 \times 50\Omega} = \frac{784}{200} = 3.92 \text{ W}$$

Maximum Power Absorbed

$$P_{max} = 3.92 \text{ W}$$

B4. i. Show how differentiation of a sinusoidal wave, leads to multiplication of $j\omega$ with the corresponding phasor of that sinusoid.

Consider a sinusoidal voltage wave in the time domain:

$$v(t) = V_m \cos(\omega t + \phi)$$

The corresponding phasor is $\mathbf{V} = V_m \angle \phi$.

Step 1: Differentiate the Sinusoid

Differentiate $v(t)$ with respect to time:

$$\frac{dv(t)}{dt} = \frac{d}{dt}[V_m \cos(\omega t + \phi)]$$

$$\frac{dv(t)}{dt} = -V_m \omega \sin(\omega t + \phi)$$

Step 2: Convert the Resulting Sinusoid into the Cosine Reference

To convert this back into a phasor, the time-domain function must be in the form of a cosine function. We use the trigonometric identity: $-\sin(\theta) = \cos(\theta + 90^\circ)$ (or $\cos(\theta + \frac{\pi}{2})$).

$$\frac{dv(t)}{dt} = V_m \omega \cos(\omega t + \phi + 90^\circ)$$

Step 3: Determine the Phasor of the Derivative

The phasor of the derivative is found by taking the magnitude and phase of the resulting cosine function:

$$\text{Phasor} \left[\frac{dv(t)}{dt} \right] = (V_m \omega) \angle (\phi + 90^\circ)$$

Using Euler's identity, a phase shift of 90° corresponds to multiplication by $e^{j90^\circ} = j$:

$$\text{Phasor} \left[\frac{dv(t)}{dt} \right] = (V_m \omega) \angle \phi \cdot 1 \angle 90^\circ$$

$$\text{Phasor} \left[\frac{dv(t)}{dt} \right] = (V_m \angle \phi) \cdot (\omega \angle 90^\circ)$$

Since $\omega \angle 90^\circ$ in polar form is equivalent to $j\omega$ in rectangular form:

$$\text{Phasor} \left[\frac{dv(t)}{dt} \right] = (V_m \angle \phi) \cdot (j\omega)$$

Since the phasor of the original sinusoid is $\mathbf{V} = V_m \angle \phi$:

$$\text{Phasor} \left[\frac{dv(t)}{dt} \right] = \mathbf{j}\omega \mathbf{V}$$

Thus, differentiation of a sinusoid in the time domain corresponds to multiplication of its phasor by $j\omega$.

B4. ii. Transform these sinusoids to phasors

$$\mathbf{a) i} = 6 \sin(50t - 40^\circ) \text{ A}$$

The phasor is derived from the cosine function. We must use the identity $\sin(\theta) = \cos(\theta - 90^\circ)$.

$$i(t) = 6 \cos(50t - 40^\circ - 90^\circ) = 6 \cos(50t - 130^\circ) \text{ A}$$

The phasor \mathbf{I} has a magnitude $I_m = 6 \text{ A}$ and phase $\phi = -130^\circ$:

$$\mathbf{I} = 6 \angle -130^\circ \text{ A}$$

$$\mathbf{b) } i = -4 \sin(30t + 50^\circ) \text{ A}$$

First, eliminate the negative sign using $-\sin(\theta) = \sin(\theta + 180^\circ)$:

$$i(t) = 4 \sin(30t + 50^\circ + 180^\circ) = 4 \sin(30t + 230^\circ) \text{ A}$$

Now, convert to cosine using $\sin(\theta) = \cos(\theta - 90^\circ)$:

$$i(t) = 4 \cos(30t + 230^\circ - 90^\circ) = 4 \cos(30t + 140^\circ) \text{ A}$$

The phasor \mathbf{I} has a magnitude $I_m = 4 \text{ A}$ and phase $\phi = 140^\circ$:

$$\mathbf{I} = 4 \angle 140^\circ \text{ A}$$

B4. iii. Determine the sum of two phasors, we calculated in B4(ii).

We need to calculate $\mathbf{I}_{\text{sum}} = \mathbf{I}_a + \mathbf{I}_b$.

Step 1: Convert Phasors to Rectangular Form

Phasor \mathbf{I}_a :

$$\mathbf{I}_a = 6 \angle -130^\circ \text{ A}$$

$$\mathbf{I}_a = 6(\cos(-130^\circ) + j \sin(-130^\circ))$$

$$\mathbf{I}_a \approx 6(-0.6428 - j0.7660) \approx -3.8568 - j4.5960 \text{ A}$$

Phasor \mathbf{I}_b :

$$\mathbf{I}_b = 4 \angle 140^\circ \text{ A}$$

$$\mathbf{I}_b = 4(\cos(140^\circ) + j \sin(140^\circ))$$

$$\mathbf{I}_b \approx 4(-0.7660 + j0.6428) \approx -3.0640 + j2.5712 \text{ A}$$

Step 2: Add the Rectangular Components

$$\mathbf{I}_{\text{sum}} = \mathbf{I}_a + \mathbf{I}_b = (-3.8568 - 3.0640) + j(-4.5960 + 2.5712)$$

$$\mathbf{I}_{\text{sum}} \approx -6.9208 - j2.0248 \text{ A}$$

Step 3: Convert the Sum back to Polar Form

Magnitude I_m :

$$I_m = \sqrt{(-6.9208)^2 + (-2.0248)^2} \approx \sqrt{47.909 + 4.100} \approx \sqrt{52.009} \approx 7.2117 \text{ A}$$

Phase ϕ : Since the real part is negative and the imaginary part is negative (Quadrant III):

$$\alpha = \tan^{-1} \left(\frac{|-2.0248|}{|-6.9208|} \right) \approx \tan^{-1}(0.2925) \approx 16.30^\circ$$

$$\phi = -180^\circ + \alpha \approx -180^\circ + 16.30^\circ = -163.70^\circ$$

or

$$\phi = 180^\circ + 16.30^\circ = 196.30^\circ$$

$$\mathbf{I}_{\text{sum}} \approx 7.212 \angle -163.7^\circ \text{ A} \quad (\text{or } 7.212 \angle 196.3^\circ \text{ A})$$

B5. i. Determine $i(t)$ in the following circuit in Figure B5.(i) using nodal analysis

The circuit components must first be converted from the time domain to the phasor domain.

Step 1: Convert to Phasor/Frequency Domain

Given the source $v_s(t) = 2 \cos(10t)$ V, the angular frequency is $\omega = 10$ rad/s.

- **Voltage Source:** $\mathbf{V}_s = 2 \angle 0^\circ$ V
- **Resistors:** $R_1 = 1\Omega$, $R_2 = 1\Omega$ (Impedance $\mathbf{Z}_R = R$)
- **Inductor:** $L = 1$ H

$$\mathbf{Z}_L = j\omega L = j(10)(1) = j10\Omega$$

- **Capacitor:** $C = 1$ F

$$\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{1}{j(10)(1)} = -j0.1\Omega$$

Step 2: Apply Nodal Analysis

Define the unknown node voltage as \mathbf{V}_1 . The 1Ω resistor on the left is in series with the voltage source, but the central 1Ω resistor is connected to the reference ground.

Apply KCL at node \mathbf{V}_1 (sum of currents leaving the node equals zero):

$$\frac{\mathbf{V}_1 - 2 \angle 0^\circ}{1} + \frac{\mathbf{V}_1}{1} + \frac{\mathbf{V}_1}{j10} + \frac{\mathbf{V}_1}{-j0.1} = 0$$

Group terms containing \mathbf{V}_1 :

$$\mathbf{V}_1 \left(\frac{1}{1} + \frac{1}{1} + \frac{1}{j10} + \frac{1}{-j0.1} \right) = \frac{2}{1}$$

$$\mathbf{V}_1 \left(2 - j\frac{1}{10} + j\frac{1}{0.1} \right) = 2$$

$$\mathbf{V}_1 (2 - j0.1 + j10) = 2$$

$$\mathbf{V}_1 (2 + j9.9) = 2$$

Step 3: Solve for \mathbf{V}_1

$$\mathbf{V}_1 = \frac{2}{2 + j9.9}$$

Convert the denominator to polar form:

$$2 + j9.9 = \sqrt{2^2 + 9.9^2} \angle \tan^{-1} \left(\frac{9.9}{2} \right) \approx 10.10 \angle 78.58^\circ$$

$$\mathbf{V}_1 = \frac{2 \angle 0^\circ}{10.10 \angle 78.58^\circ} \approx 0.198 \angle -78.58^\circ \text{ V}$$

Step 4: Solve for i

The current i is the current flowing through the central 1Ω resistor, which is $\frac{\mathbf{V}_1}{1\Omega}$.

$$\mathbf{I} = \frac{\mathbf{V}_1}{1\Omega} \approx 0.198 \angle -78.58^\circ \text{ A}$$

Step 5: Convert back to Time Domain

The time domain current $i(t)$ is:

$$i(t) = 0.198 \cos(10t - 78.58^\circ) \text{ A}$$

B5. ii. Determine voltage V_0 in the following circuit in Figure B5.(ii) using mesh analysis

The circuit is already in the phasor domain. We define three mesh currents, \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 (clockwise).

Step 1: Define Mesh Equations (Phasor Domain)

Mesh 1 (Contains current source): The $4\angle 0^\circ$ A current source dictates the relationship between \mathbf{I}_1 and \mathbf{I}_3 :

$$\mathbf{I}_1 - \mathbf{I}_3 = 4\angle 0^\circ \text{ A}$$

Mesh 2 (No source, KVL):

$$(8)\mathbf{I}_2 + (15)(\mathbf{I}_2 - \mathbf{I}_3) = 0$$

$$23\mathbf{I}_2 - 15\mathbf{I}_3 = 0 \quad (\text{Eq. 2})$$

Mesh 3 (Contains voltage source and current source, KVL):

$$(12)(\mathbf{I}_3 - \mathbf{I}_1) + (15)(\mathbf{I}_3 - \mathbf{I}_2) + 10\angle 0^\circ = 0$$

$$-12\mathbf{I}_1 - 15\mathbf{I}_2 + (12 + 15)\mathbf{I}_3 = -10$$

$$-12\mathbf{I}_1 - 15\mathbf{I}_2 + 27\mathbf{I}_3 = -10 \quad (\text{Eq. 3})$$

Step 2: Solve the System of Equations

From Eq. 1: $\mathbf{I}_1 = 4 + \mathbf{I}_3$.

Substitute \mathbf{I}_1 into Eq. 3:

$$-12(4 + \mathbf{I}_3) - 15\mathbf{I}_2 + 27\mathbf{I}_3 = -10$$

$$-48 - 12\mathbf{I}_3 - 15\mathbf{I}_2 + 27\mathbf{I}_3 = -10$$

$$15\mathbf{I}_3 - 15\mathbf{I}_2 = 38 \quad (\text{Eq. 4})$$

From Eq. 2: $\mathbf{I}_2 = \frac{15}{23}\mathbf{I}_3$.

Substitute \mathbf{I}_2 into Eq. 4:

$$15\mathbf{I}_3 - 15\left(\frac{15}{23}\mathbf{I}_3\right) = 38$$

$$15\mathbf{I}_3\left(1 - \frac{15}{23}\right) = 38$$

$$15\mathbf{I}_3\left(\frac{23 - 15}{23}\right) = 38$$

$$15\mathbf{I}_3\left(\frac{8}{23}\right) = 38 \implies \mathbf{I}_3 = \frac{38 \times 23}{15 \times 8} = \frac{874}{120} \approx 7.283 \text{ A}$$

Step 3: Determine V_0

The voltage V_0 is the voltage across the 8Ω resistor, which is $V_0 = 8I_2$. First, find I_2 :

$$I_2 = \frac{15}{23}I_3 = \frac{15}{23} \times \frac{874}{120} = \frac{15 \times 874}{23 \times 120} = \frac{13110}{2760} = \frac{485}{92} \approx 5.272 \text{ A}$$

Now, find V_0 :

$$V_0 = 8I_2 = 8 \times \frac{485}{92} = \frac{3880}{92} = \frac{970}{23}$$

$$V_0 \approx 42.174\angle 0^\circ \text{ V}$$

(Since all sources and impedances are real, the voltage V_0 is real and has a phase of 0°).

B6. i. Use superposition theorem to find i_o in the following circuit in Figure B6.(i).

The circuit has two independent sources: a current source $I_s = 1\angle 0^\circ \text{ A}$ and a voltage source $V_s = 20\angle 90^\circ \text{ V}$. We find the load current i_o (through the $j10\Omega$ inductor) by summing the results from two separate cases.

Step 1: Define Impedances (Phasor Domain)

The circuit components are given as steady-state impedances:

- Resistors: $R_1 = 4\Omega$, $R_2 = 20\Omega$, $R_3 = 1\Omega$
- Inductor: $Z_L = j10\Omega$
- Capacitor: $Z_C = -j5\Omega$

Case 1: $1\angle 0^\circ \text{ A}$ Current Source Active, V_s Shorted (i'_o)

The voltage source is short-circuited. The 4Ω resistor is now in parallel with the 1Ω resistor.

1. **Equivalent Impedance (R_{eq}):** The 4Ω and 1Ω resistors are in parallel due to the short circuit.

$$R_{eq} = 4\Omega || 1\Omega = \frac{4 \times 1}{4 + 1} = 0.8\Omega$$

2. **Impedance of the Load Branch (Z_{loop}):** The current flows through R_{eq} , Z_L , and Z_C in series.

$$Z_{loop} = R_{eq} + Z_L + Z_C = 0.8 + j10 - j5 = 0.8 + j5\Omega$$

3. **Current Divider Rule (CDR):** The $1\angle 0^\circ$ A current splits between the 20Ω resistor and \mathbf{Z}_{loop} . The current flowing into the loop is \mathbf{i}'_o :

$$\mathbf{i}'_o = 1\angle 0^\circ \cdot \frac{R_2}{R_2 + \mathbf{Z}_{loop}} = \frac{20}{20 + 0.8 + j5} = \frac{20}{20.8 + j5}$$

4. **Calculation:** Convert the denominator to polar form: $20.8 + j5 \approx 21.39\angle 13.5^\circ$.

$$\mathbf{i}'_o \approx \frac{20\angle 0^\circ}{21.39\angle 13.5^\circ} \approx \mathbf{0.935\angle -13.5^\circ} \text{ A}$$

Case 2: $20\angle 90^\circ$ V Voltage Source Active, \mathbf{I}_s Opened (\mathbf{i}''_o)

The current source is replaced by an open circuit, disconnecting the 20Ω resistor.

1. **Total Loop Impedance (\mathbf{Z}_{total}):** The components R_1 , R_3 , \mathbf{Z}_L , and \mathbf{Z}_C are now in series with \mathbf{V}_s .

$$\mathbf{Z}_{total} = R_1 + R_3 + \mathbf{Z}_L + \mathbf{Z}_C = 4 + 1 + j10 - j5 = 5 + j5\Omega$$

2. **Loop Current (\mathbf{i}''_o):** The current is found using Ohm's Law.

$$\mathbf{i}''_o = \frac{\mathbf{V}_s}{\mathbf{Z}_{total}} = \frac{20\angle 90^\circ}{5 + j5}$$

3. **Calculation:** Convert the denominator to polar form: $5 + j5 \approx 7.071\angle 45^\circ$.

$$\mathbf{i}''_o = \frac{20\angle 90^\circ}{7.071\angle 45^\circ} \approx \mathbf{2.828\angle 45^\circ} \text{ A}$$

Step 3: Total Current \mathbf{i}_o

The total current is the phasor sum $\mathbf{i}_o = \mathbf{i}'_o + \mathbf{i}''_o$.

1. **Convert to Rectangular Form:**

$$\mathbf{i}'_o \approx 0.935 \cos(-13.5^\circ) + j0.935 \sin(-13.5^\circ) \approx 0.908 - j0.218 \text{ A}$$

$$\mathbf{i}''_o \approx 2.828 \cos(45^\circ) + j2.828 \sin(45^\circ) \approx 2.000 + j2.000 \text{ A}$$

2. **Summation:**

$$\mathbf{i}_o \approx (0.908 + 2.000) + j(-0.218 + 2.000) \approx 2.908 + j1.782 \text{ A}$$

3. **Final Polar Form:**

$$I_m = \sqrt{2.908^2 + 1.782^2} \approx 3.41 \text{ A}$$

$$\phi = \tan^{-1}\left(\frac{1.782}{2.908}\right) \approx 31.46^\circ$$

Final Answer

$$\mathbf{i}_o \approx 3.41 \angle 31.46^\circ \text{ A}$$

B6. ii. At $\omega = 10^3 \text{ rad/s}$ find the input admittance of the following circuit in Figure B6.(ii).

The input admittance, \mathbf{Y}_{in} , is the reciprocal of the total input impedance, \mathbf{Z}_{in} , where \mathbf{Z}_{in} is the series combination of the capacitor \mathbf{Z}_C and the equivalent parallel impedance \mathbf{Z}_{eq} .

Step 1: Calculate Impedances at $\omega = 10^3 \text{ rad/s}$

The circuit contains a capacitor ($C=20 \mu\text{F}$) and an inductor ($L=10 \text{ mH}$).

1. Capacitor Impedance (\mathbf{Z}_C): (Series component)

$$\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{1}{j(10^3)(20 \times 10^{-6})} = \frac{1}{j(0.02)} = -j50\Omega$$

2. Inductor Impedance (\mathbf{Z}_L):

$$\mathbf{Z}_L = j\omega L = j(10^3)(10 \times 10^{-3}) = j10\Omega$$

Step 2: Calculate Equivalent Admittance (\mathbf{Y}_{eq})

The parallel section, \mathbf{Z}_{eq} , consists of three main branches connected from the central top node to the bottom reference node. We assume the structure is a parallel combination of 30Ω , 60Ω , and the series combination of 40Ω and \mathbf{Z}_L .

$$\mathbf{Y}_{\text{eq}} = \frac{1}{30} + \frac{1}{60} + \frac{1}{40 + \mathbf{Z}_L}$$

1. Admittance of Resistors (\mathbf{Y}_R):

$$\mathbf{Y}_R = \frac{1}{30} + \frac{1}{60} = \frac{2+1}{60} = \frac{3}{60} = 0.05 \text{ S}$$

2. Admittance of \mathbf{Z}_{40+L} (\mathbf{Y}_L):

$$\mathbf{Y}_L = \frac{1}{40 + j10} = \frac{1}{40 + j10} \times \frac{40 - j10}{40 - j10} = \frac{40 - j10}{1600 + 100} = \frac{40 - j10}{1700}$$

$$\mathbf{Y}_L \approx 0.02353 - j0.00588 \text{ S}$$

3. Total Parallel Admittance (\mathbf{Y}_{eq}):

$$\mathbf{Y}_{\text{eq}} = \mathbf{Y}_R + \mathbf{Y}_L \approx 0.05 + 0.02353 - j0.00588$$

$$\mathbf{Y}_{\text{eq}} \approx 0.07353 - j0.00588 \text{ S}$$

This is an exclusive content of Academizz. To get access to more resources, subscribe to Academizz(app.academizz.com).

Step 3: Calculate Total Input Impedance (\mathbf{Z}_{in})

$$\mathbf{Z}_{eq} = \frac{1}{\mathbf{Y}_{eq}} = \frac{1}{0.07353 - j0.00588}$$

$$\mathbf{Z}_{eq} \approx 13.516 + j1.081\Omega$$

The total input impedance \mathbf{Z}_{in} is the series combination of \mathbf{Z}_C and \mathbf{Z}_{eq} :

$$\mathbf{Z}_{in} = \mathbf{Z}_C + \mathbf{Z}_{eq} = -j50 + (13.516 + j1.081)$$

$$\mathbf{Z}_{in} \approx 13.516 - j48.919\Omega$$

Step 4: Calculate Input Admittance (\mathbf{Y}_{in})

$$\mathbf{Y}_{in} = \frac{1}{\mathbf{Z}_{in}} = \frac{1}{13.516 - j48.919}$$

Rationalize the denominator:

$$\mathbf{Y}_{in} = \frac{1}{13.516 - j48.919} \times \frac{13.516 + j48.919}{13.516 + j48.919}$$

$$\mathbf{Y}_{in} = \frac{13.516 + j48.919}{(13.516)^2 + (48.919)^2} \approx \frac{13.516 + j48.919}{2575.7}$$

$$\mathbf{Y}_{in} \approx 0.00525 + j0.0190 \text{ S}$$

Final Answer in Polar Form (Optional)

$$\mathbf{Y}_{in} \approx \sqrt{0.00525^2 + 0.0190^2} \angle \tan^{-1} \left(\frac{0.0190}{0.00525} \right)$$

$$\mathbf{Y}_{in} \approx \mathbf{0.0197} \angle \mathbf{74.55^\circ} \text{ S}$$

B7. i. Find v_o of the circuit shown in Figure B7.(i) using superposition theorem.

The circuit has three independent sources operating at three different frequencies:

- $\mathbf{V}_{s1} : 10 \cos(2t) \text{ V} \implies \omega_1 = 2 \text{ rad/s}$
- $\mathbf{I}_{s2} : 2 \sin(5t) \text{ A} \implies \omega_2 = 5 \text{ rad/s}$
- $\mathbf{V}_{s3} : 5 \text{ V (DC)} \implies \omega_3 = 0 \text{ rad/s}$

The total output voltage is the sum of the time-domain components:

$v_o(t) = v_{o1}(t) + v_{o2}(t) + v_{o3}(t)$. We define the output voltage as $\mathbf{V}_o = \mathbf{V}_a - \mathbf{V}_b$, where \mathbf{V}_a is the node voltage between the inductor (2 H) and the resistor (1 Ω), and \mathbf{V}_b is the node voltage between the resistor (1 Ω) and the capacitor (0.1 F).

Case 1: $10 \cos(2t)$ V Source Active ($\omega_1 = 2$ rad/s)

$\mathbf{V}_{s1} = 10 \angle 0^\circ$ V. \mathbf{I}_{s2} is opened, \mathbf{V}_{s3} is shorted.

Impedances at $\omega_1 = 2$:

- $\mathbf{Z}_{L1} = j\omega_1 L = j(2)(2) = j4\Omega$
- $\mathbf{Z}_{C1} = \frac{1}{j\omega_1 C} = \frac{1}{j(2)(0.1)} = -j5\Omega$

Applying Nodal Analysis at \mathbf{V}_a and \mathbf{V}_b (with \mathbf{V}_{s3} shorted, 4Ω is to ground):

$$\text{KCL at } \mathbf{V}_a : \frac{\mathbf{V}_a - 10}{j4} + \frac{\mathbf{V}_a - \mathbf{V}_b}{1} = 0 \implies \mathbf{V}_a(1 - j0.25) - \mathbf{V}_b = -j2.5$$

$$\text{KCL at } \mathbf{V}_b : \frac{\mathbf{V}_b - \mathbf{V}_a}{1} + \frac{\mathbf{V}_b}{-j5} + \frac{\mathbf{V}_b}{4} = 0 \implies -\mathbf{V}_a + \mathbf{V}_b(1.25 + j0.2) = 0$$

Solving the system of equations yields $\mathbf{V}_{o1} = \mathbf{V}_a - \mathbf{V}_b$:

$$\mathbf{V}_{o1} \approx 2.013 - j1.664 \text{ V} \approx 2.61 \angle -39.55^\circ \text{ V}$$

$$v_{o1}(t) \approx 2.61 \cos(2t - 39.55^\circ) \text{ V}$$

Case 2: $2 \sin(5t)$ A Source Active ($\omega_2 = 5$ rad/s)

$\mathbf{I}_{s2} = 2 \angle -90^\circ = -j2$ A. \mathbf{V}_{s1} and \mathbf{V}_{s3} are shorted.

Impedances at $\omega_2 = 5$:

- $\mathbf{Z}_{L2} = j\omega_2 L = j(5)(2) = j10\Omega$
- $\mathbf{Z}_{C2} = \frac{1}{j\omega_2 C} = \frac{1}{j(5)(0.1)} = -j2\Omega$

Applying Nodal Analysis (\mathbf{V}_{s1} shorted, \mathbf{V}_{s3} shorted):

$$\text{KCL at } \mathbf{V}_a : \frac{\mathbf{V}_a}{j10} + \frac{\mathbf{V}_a - \mathbf{V}_b}{1} = -(-j2) \implies \mathbf{V}_a(1 - j0.1) - \mathbf{V}_b = j2$$

$$\text{KCL at } \mathbf{V}_b : \frac{\mathbf{V}_b - \mathbf{V}_a}{1} + \frac{\mathbf{V}_b}{-j2} + \frac{\mathbf{V}_b}{4} = 0 \implies -\mathbf{V}_a + \mathbf{V}_b(1.25 + j0.5) = 0$$

Solving the system of equations yields $\mathbf{V}_{o2} = \mathbf{V}_a - \mathbf{V}_b$:

$$\mathbf{V}_{o2} \approx -0.488 + j2.2765 \text{ V} \approx 2.328 \angle 102.08^\circ \text{ V}$$

Converting back to the time domain (cosine reference):

$$v_{o2}(t) \approx 2.328 \cos(5t + 102.08^\circ) \text{ V}$$

Case 3: 5 V DC Source Active ($\omega_3 = 0$)

\mathbf{V}_{s1} is shorted, \mathbf{I}_{s2} is opened.

- $\mathbf{Z}_{L3} = 0\Omega$ (short circuit)
- $\mathbf{Z}_{C3} = \infty\Omega$ (open circuit)

The shorted inductor (in series with the shorted \mathbf{V}_{s1}) connects \mathbf{V}_a directly to the ground reference. Thus, $\mathbf{V}_a = 0$ V. The open capacitor forces the current in the right loop (containing 1Ω , 4Ω , and 5 V) to zero.

$$\text{KCL at } \mathbf{V}_b : \frac{\mathbf{V}_b - \mathbf{V}_a}{1} + i_C = 0$$

Since $\mathbf{V}_a = 0$ and $i_C = 0$, this requires $\mathbf{V}_b = 0$ V.

$$v_{o3} = \mathbf{V}_a - \mathbf{V}_b = 0 - 0 = 0 \text{ V}$$

Final Summation

$$v_o(t) = v_{o1}(t) + v_{o2}(t) + v_{o3}(t)$$
$$v_o(t) \approx 2.61 \cos(2t - 39.55^\circ) + 2.328 \cos(5t + 102.08^\circ) \text{ V}$$

B7. ii. Obtain the Thevenin impedance at terminals a-b of the following circuit in Figure B7.(ii).

To find the Thevenin impedance (\mathbf{Z}_{Th}), we replace the independent voltage source ($\mathbf{V}_s = 120\angle 75^\circ$ V) with a short circuit. The terminals 'a' and 'b' are within a bridge network, and the source is connected across the input terminals of the bridge ('d' and 'c').

Step 1: Simplify the Circuit

When the source \mathbf{V}_s is shorted, terminals 'd' and 'c' are connected together.

- Impedance $\mathbf{Z}_1 = -j6\Omega$ (between d and a) is in parallel with $\mathbf{Z}_3 = 8\Omega$ (between c and a).
- Impedance $\mathbf{Z}_2 = 4\Omega$ (between d and b) is in parallel with $\mathbf{Z}_4 = j12\Omega$ (between c and b).

The Thevenin impedance \mathbf{Z}_{Th} seen between a and b is the series combination of these two parallel groups:

$$\mathbf{Z}_{Th} = (\mathbf{Z}_1 || \mathbf{Z}_3) + (\mathbf{Z}_2 || \mathbf{Z}_4)$$

Step 2: Calculate $Z_{a,c/d}$

$$\mathbf{Z}_{ac} = \mathbf{Z}_1 || \mathbf{Z}_3 = \frac{(-j6)(8)}{-j6 + 8} = \frac{-j48}{8 - j6}$$
$$\mathbf{Z}_{ac} = \frac{-j48}{8 - j6} \times \frac{8 + j6}{8 + j6} = \frac{-j384 + 288}{64 + 36} = \frac{288 - j384}{100}$$
$$\mathbf{Z}_{ac} = 2.88 - j3.84\Omega$$

Step 3: Calculate $Z_{b,c/d}$

$$\mathbf{Z}_{bc} = \mathbf{Z}_2 || \mathbf{Z}_4 = \frac{(4)(j12)}{4 + j12} = \frac{j48}{4 + j12}$$
$$\mathbf{Z}_{bc} = \frac{j48}{4 + j12} \times \frac{4 - j12}{4 - j12} = \frac{j192 + 576}{16 + 144} = \frac{576 + j192}{160}$$
$$\mathbf{Z}_{bc} = \frac{384}{160} + j\frac{192}{160} = 3.6 + j1.2\Omega$$

Step 4: Calculate Z_{Th}

$$\mathbf{Z}_{Th} = \mathbf{Z}_{ac} + \mathbf{Z}_{bc} = (2.88 - j3.84) + (3.6 + j1.2)$$
$$\mathbf{Z}_{Th} = (2.88 + 3.6) + j(-3.84 + 1.2)$$
$$\mathbf{Z}_{Th} = \mathbf{6.48 - j2.64}\square$$